

# 7447 BCD - Seven segment Display Decoder Assignment

Peravali Bhavana Durga  
Roll No: FWC22278  
bhavanadurgaperavali@gmail.com

## I. ABSTRACT

This paper shows how to use the 7447 BCD-Seven segment Display Decoder to learn Boolean logic using arduino uno.

## II. COMPONENTS

The required components list is given in Table: I. and seven segment display is shown in Fig.2 and IC 7447 diagram is shown in Fig.1.

Components	Value	Quantity
IC	7447	1
seven segment display		1
Arduino	UNO	1
Jumper Wires		10
Breadboard		1

TABLE I



Fig. 1.

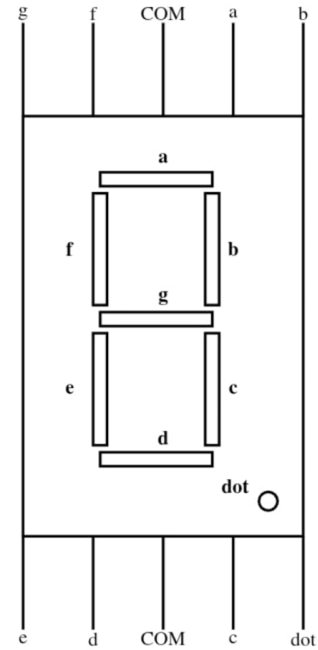


Fig. 2.

## III. PROCEDURE

- 1) Make the connections of 7447 IC and seven segment display as per below Fig.3.

7447	$\bar{a}$	$\bar{b}$	$\bar{c}$	$\bar{d}$	$\bar{e}$	$\bar{f}$	$\bar{g}$
Display	a	b	c	d	e	f	g

Fig. 3.

- 2) Make the connections of 7447 IC and arduino uno as per below Fig.4.

<b>7447</b>	D	C	B	A
<b>Arduino</b>	5	4	3	2

Fig. 4.

- 3) Truth Table for incrementing from 0 to 9 in seven segment display

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE II

- 4) Execute the arduino code without any errors.
- 5) After upload the code into hardware setup using arduino IDE platform with hex file.

#### IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.5.
- 2) <https://github.com/rajib05ra/FWC-Assignments/tree/main/Assignment>

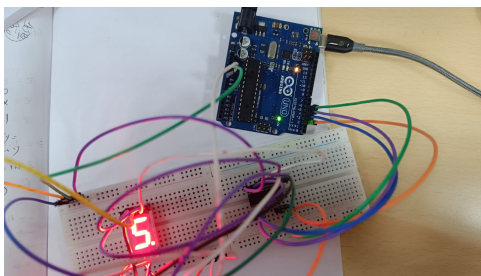


Fig. 5.

#### V. CONCLUSION

Hence implementation of 7447 IC, Seven segment display using arduino UNO is done.